

1434**Code : 15MC42T**Register
Number

--	--	--	--	--	--	--

IV Semester Diploma Examination, April/May-2018**INDUSTRIAL ELECTRONICS****Time : 3 Hours]****[Max. Marks : 100****Published By:****PART - A**Answer any **six** questions :**5 × 6 = 30**

1. Explain the working and characteristics of DIAC. **5**
2. Explain step down chopper. **5**
3. Explain ladder diagram with an example. **5**
4. Explain in-plant distribution with diagram. **5**
5. Explain the following mechanically operated switch with neat diagram. **5**
 - (a) Float switch
 - (b) Pressure switch
6. Explain solid state relays. **5**
7. Explain pneumatic timer. **5**
8. Explain the characteristics of servo motor. **5**
9. Explain the operation of Brushless DC motor. **5**

PART – B

Answer any **seven** full questions :

10 × 7 = 70

10. Explain the construction, working, characteristics of SCR. 10
11. Explain the working of Full wave controlled rectifier. 10
12. Explain UPS with a neat block diagram. 10
13. Explain the following manually operated switch with neat diagram. 10
- (a) Toggle switch
 - (b) Push button
 - (c) Slide switch
 - (d) Rotary switch
 - (e) Thumb wheel switch
14. Explain Magnetic Motor Starter. 10
15. Explain the operation of solenoid. 10
16. Explain the variable frequency AC drive system. 10
17. Explain the methods to control the speed of DC motor. 10
18. Develop the control circuit and load circuit for motor starter using on/off switch using three wire method. 10
19. Develop the control circuit and load circuit for motor to move in jogging / inching both in clockwise & anticlockwise direction. 10